

# COMP2611: Computer Organization

## Arithmetic Logic Unit

# Arithmetic Logic Unit

## Review of the 1-bit ALU

- 1-bit ALU
- 1-bit ALU for the MSB
- Overflow detection



## An extended 32-bit ALU

- Ripple carry Add/Sub
- SLT implementation
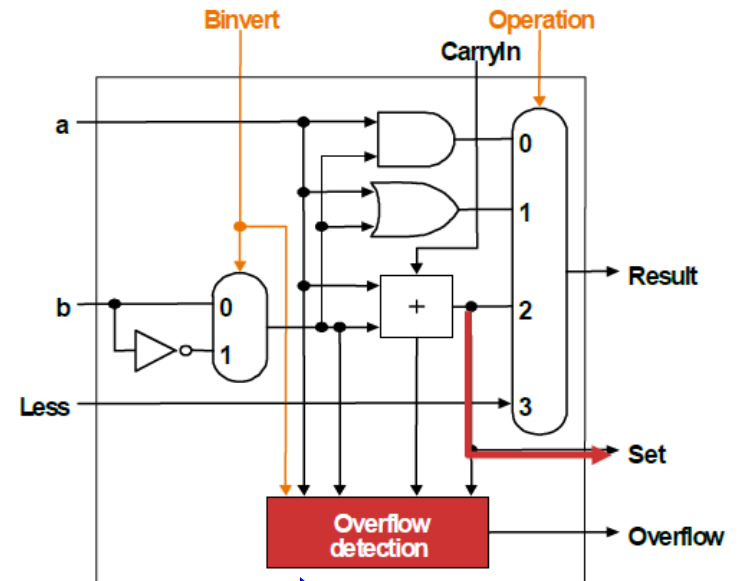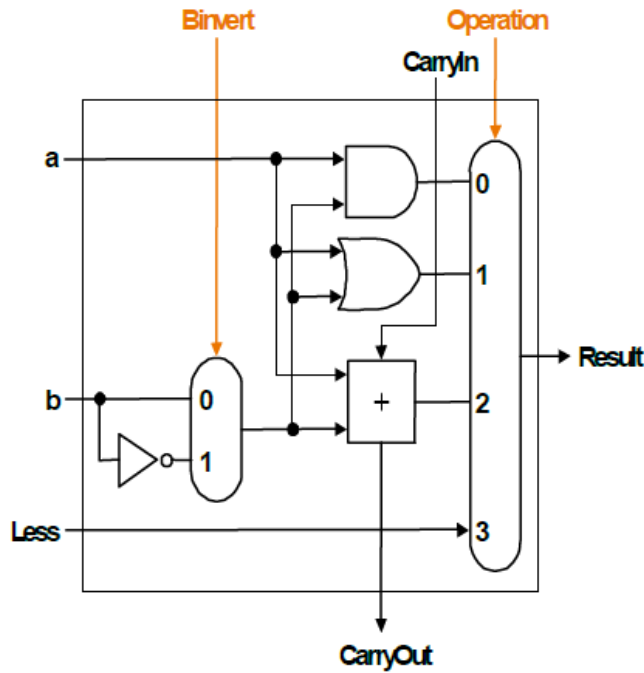
## Exercises

A 32-bit ALU can be constructed using the following 1-bit ALUs

- ❑ 1-bit ALU for bits 0 to 30
- ❑ 1-bit ALU for the Most Significant Bit (MSB):



Overflow conditions

Operation	Sign Bit of X	Sign Bit of Y	Sign Bit of Result
X + Y	0	0	1
X + Y	1	1	0
X - Y	0	1	1
X - Y	1	0	0

# Arithmetic Logic Unit

Review of the 1-bit ALU

- 1-bit ALU
- ALU for the MSB
- Overflow detection


An extended 32-bit ALU

- Ripple carry Add/Sub
- SLT implementation

Exercises
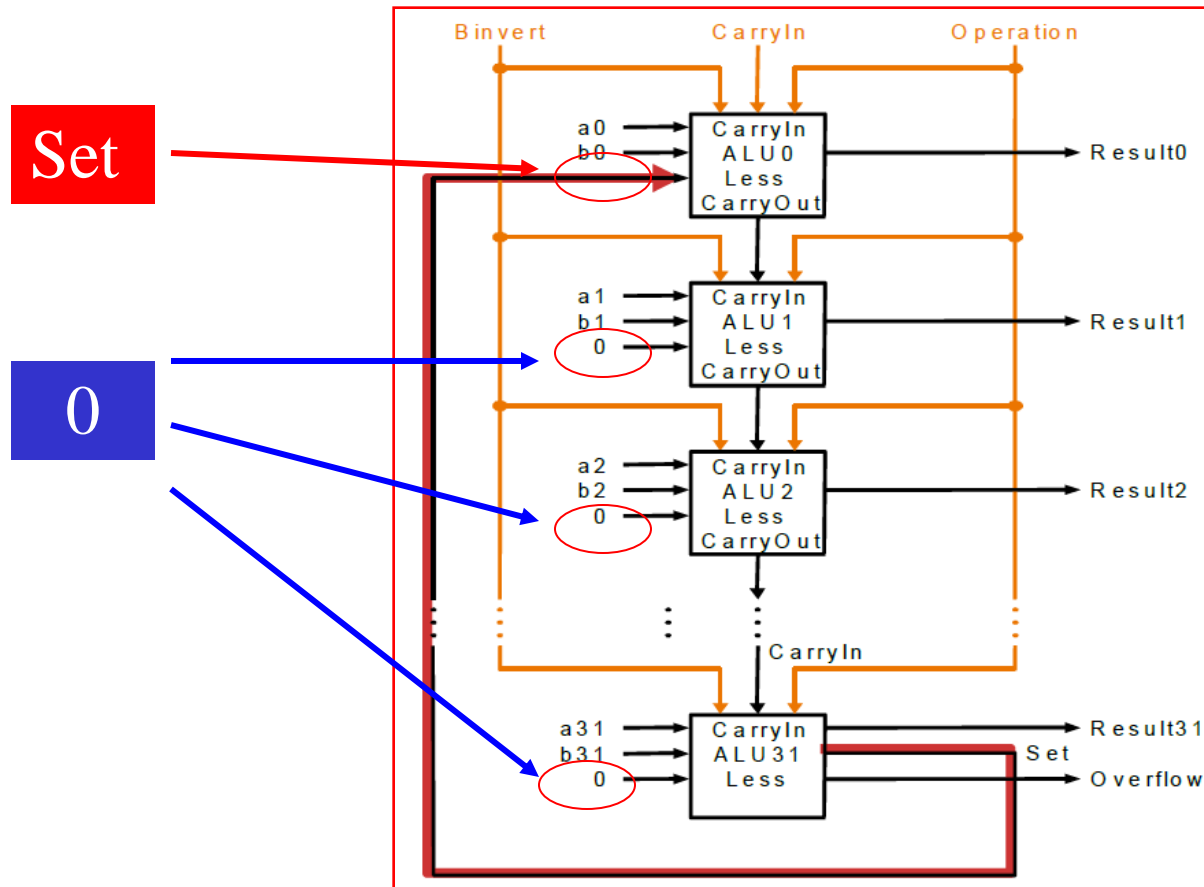
# A 32-bit ALU that supports ADD, SUB, AND, OR, SLT 5

- An extended 32-bit ALU (supports SLT) can be formed by connecting 32 1-bit ALUs as follows. Note the 0's at the "Less" input for ALU1-ALU31, note also the **set** signal from ALU31 to ALU0.



# Arithmetic Logic Unit

Review of the 1-bit ALU

- 1-bit ALU
- ALU for the MSB
- Overflow detection

An extended 32-bit ALU

- Ripple carry Add/Sub
- SLT implementation

**Exercises**

**Question 1:** By referring to slides 4 and 5, explain how SLT operation can be performed. State the values for the control signals **Binvert**, **CarryIn** and **Operation**.

**Question 2:** By referring to slides 4 and 5, derive the logic expression in the Sum of Product form (SoP) for overflow conditions.



**Question 3:** The SLT operation depends on the result of  $A-B$ , and set whenever the sign bit of the operation is asserted. Describe a scenario such that this approach does not work correctly.

**Question 4:** By referring to the modified 32-bit ALU below, explain how the condition  $A==B$  is detected. State the values for the control signals **Bnegate** and **Operation**.

